

# TPA31xxDx Bootstrap Circuit

ShawnZheng

## ABSTRACT

The full H-bridge output stages use only n-channel MOSFETs (NMOS) on TPA31xx devices. Therefore, bootstrap capacitors are required to correctly turn on the high side of each output. This document introduces this circuit on TPA31xxDx devices.

---

**NOTE:** This document only applies for TPA31xxDx devices.

---

## Contents

1	Introduction .....	2
2	Device Overview .....	2
3	Application Considerations .....	3
	3.1 PWM Switching Frequency and Duty-Cycle .....	4
	3.2 Load Resistance .....	6
	3.3 Input Signal Frequency .....	6
	3.4 PVCC.....	7
4	Conclusion .....	7

## List of Figures

1	Bootstrap Capacitor Charging.....	2
2	Bootstrap Capacitor Discharging .....	2
3	Bootstrap Voltage With $F_{sw} = 1$ MHz (PVCC = 20 V, Open Load, $F_{IN} = 10$ Hz, $V_{IN} = 900$ mVrms, Gain = 26 dB) .....	3
4	Output Duty-Cycle With $F_{sw} = 400$ kHz (PVCC = 20 V, Open Load, $F_{IN} = 50$ Hz, $V_{IN} = 680$ mVrms, Gain = 26 dB) .....	4
5	Output Duty-Cycle With $F_{sw} = 1.2$ MHz (PVCC = 20 V, Open Load, $F_{IN} = 50$ Hz, $V_{IN} = 680$ mVrms, Gain = 26 dB) .....	5
6	Output Duty-Cycle With $F_{sw} = 400$ kHz (PVCC = 20 V, Open Load, $F_{IN} = 50$ Hz, $V_{IN} = 300$ mVrms, Gain = 26 dB) .....	5
7	Slew Rate of Output PWM .....	6
8	Output PWM With $F_{IN} = 50$ Hz (PVCC = 20 V, Open Load, $F_{sw} = 1.2$ MHz, $V_{IN} = 600$ mVrms, Gain = 26 dB)..	6
9	Output PWM With $F_{IN} = 1$ kHz (PVCC=20V, Open Load, $F_{sw}=1.2$ MHz, $V_{IN}=600$ mVrms, Gain=26dB) .....	7
10	Capacitance Equivalent Circuit .....	7

## List of Tables

## Trademarks

All trademarks are the property of their respective owners.

## 1 Introduction

In most switching applications, the bootstrap circuit is widely used to drive the high-side metal-oxide-semiconductor field-effect transistor (MOSFET). This bootstrap circuit technique has the advantage of being simple and low cost. The bootstrap capacitors connected between the BSxx pins and corresponding output pins function as a floating power supply for the high-side N-channel power MOSFET gate drive circuitry. During each high-side switching cycle, the bootstrap capacitors hold the gate-to-source voltage high enough to keep the high-side MOSFETs turned on.

The purpose of this application note is to demonstrate in detail how the bootstrap circuit works on TP31xxDx devices, which are high-performance, class-D, audio amplifiers and application considerations which users must pay attention to are also included.

## 2 Device Overview

P-channel MOSFETs (PMOS) are typically approximately 3x larger than NMOS with the same  $R_{DS(on)}$ . To reduce the die area, replace the high-side PMOS device with NMOS. An all-NMOS output stage requires a bootstrap supply to power the high-side gate driver. The bootstrap diode forward biases while the output is low, to charge the bootstrap capacitor from GVDD. The bootstrap capacitor holds the bootstrap node at  $OUT+ GVDD$ . The bootstrap diode reverse biases when the output goes high. This process provides a floating power source for the high-side Gate Drive.

The bootstrap circuit is useful in a high-voltage gate driver and operates as follows. When OUT is pulled down to ground (the low-side switch is turned on and the high-side switch is turned off), the bootstrap capacitor charges through the bootstrap diode from the GVDD power supply, as shown in Figure 1. When the high-side switch is turned on and the low-side switch is turned off, OUT is pulled up to PVCC, then the bootstrap diode reverses bias and blocks the rail voltage from GVDD, as shown in Figure 2.

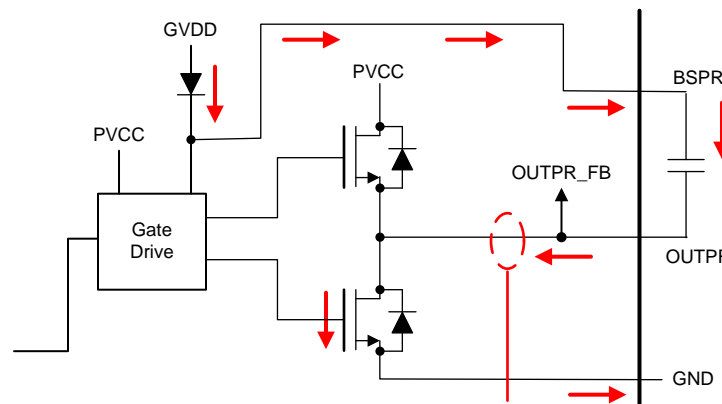


Figure 1. Bootstrap Capacitor Charging


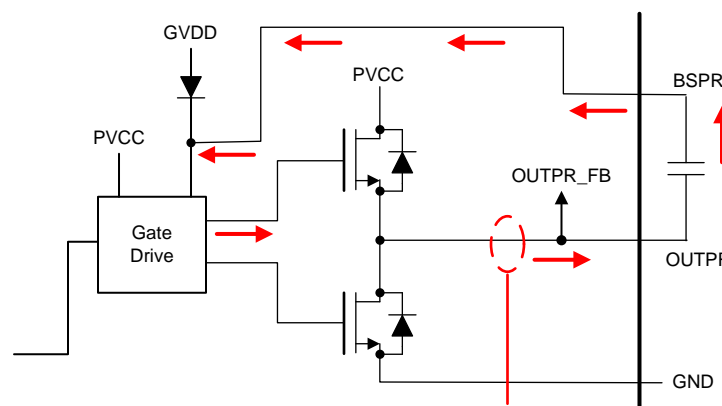


Figure 2. Bootstrap Capacitor Discharging

### 3 Application Considerations

The bootstrap circuit has the advantage of being both simple and low-cost. However, the requirement to refresh the charge on the bootstrap capacitor may result in some limitations. The following [Figure 3](#) shows a failed case, which is caused by over-discharging on bootstrap capacitors. The red waveform in the following picture is for BSPR, the blue one is for OUTPR, and the green one is for FAULT. It is safe if the voltage difference between BSPR and OUTPT is larger than 5 V. From this screen capture, we can see that the FAULT is triggered because the voltage difference decreases to around 3 V. This measurement is based on 1-MHz switching frequency and 0.22- $\mu$ F bootstrap capacitors.

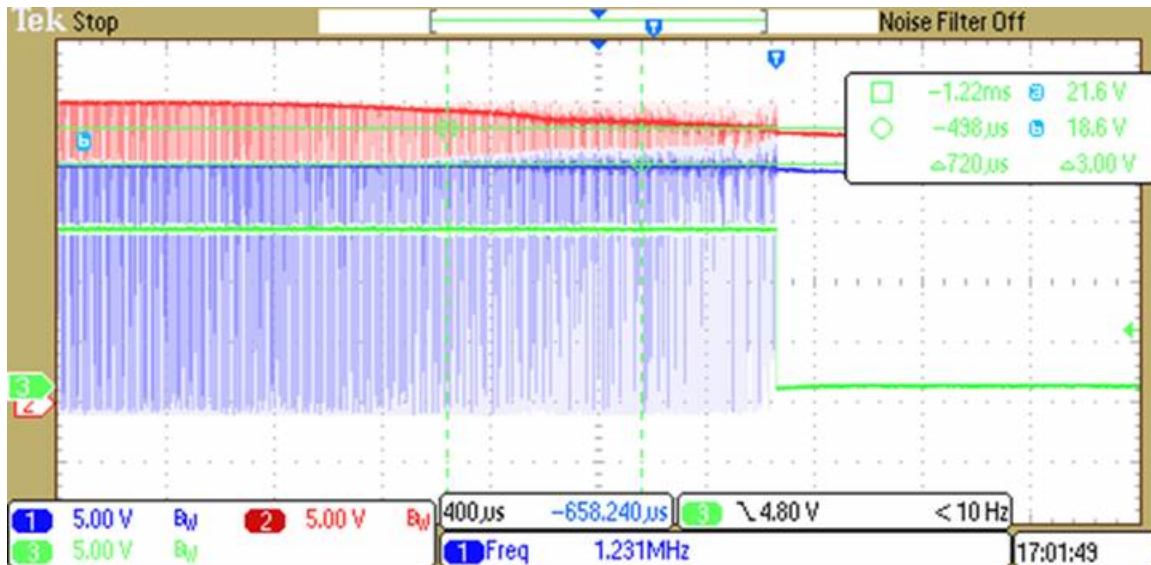


**Figure 3. Bootstrap Voltage With  $F_{sw} = 1$  MHz**  
(PVCC = 20 V, Open Load,  $F_{IN} = 10$  Hz,  $V_{IN} = 900$  mVrms, Gain = 26 dB)

In the following sections, some conditions that could cause this issue are introduced.

### 3.1 PWM Switching Frequency and Duty-Cycle

The charging time for the bootstrap capacitors is shorter for the high-PWM switching frequency than the low-PWM switching frequency case. The charge time is even shorter for the high-PWM duty-cycle case (the output signal is high). There is a probability that the voltage across the bootstrap capacitors is too low to turn on the high-side MOSFET.

Figure 4 shows the case with 400-kHz PWM frequency and Figure 5 shows the case with 1.2-MHz PWM frequency. Apparently, the charging time in each PWM cycle is shorter with higher PWM frequency. Figure 4 shows a 680-mVrms input signal, Figure 6 shows 300 mV, and all of the other conditions are the same. Apparently, the latter one has a longer charging time for the bootstrap capacitors.

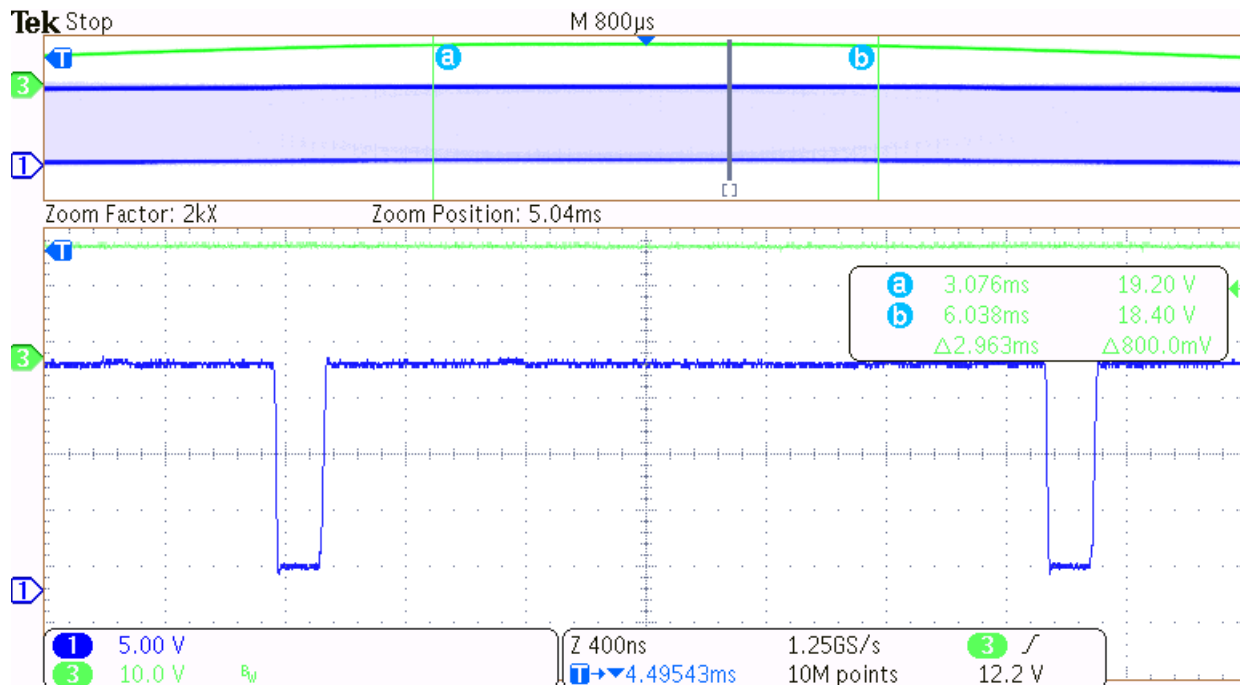

**Figure 4. Output Duty-Cycle With  $F_{sw} = 400$  kHz**  
(PVCC = 20 V, Open Load,  $F_{in} = 50$  Hz,  $V_{in} = 680$  mVrms, Gain = 26 dB)

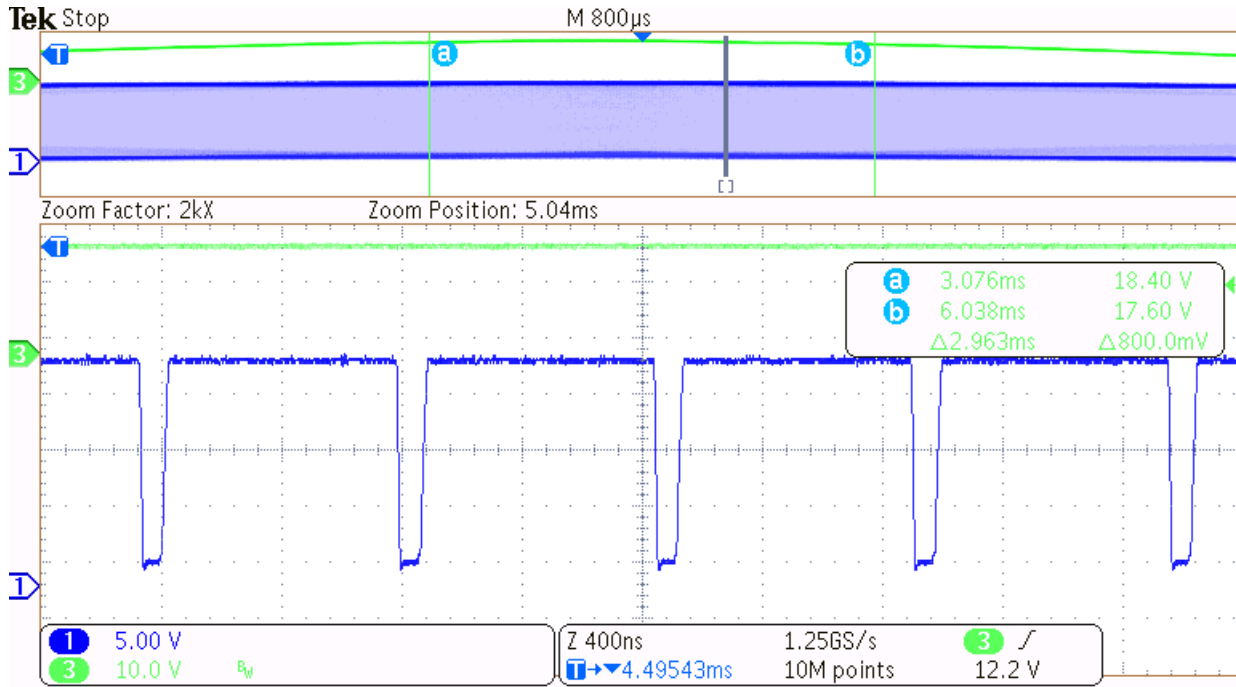


Figure 5. Output Duty-Cycle With  $F_{sw} = 1.2 \text{ MHz}$   
(PVCC = 20 V, Open Load,  $F_{IN} = 50 \text{ Hz}$ ,  $V_{IN} = 680 \text{ mVrms}$ , Gain = 26 dB)

 


Figure 6. Output Duty-Cycle With  $F_{sw} = 400 \text{ kHz}$   
(PVCC = 20 V, Open Load,  $F_{IN} = 50 \text{ Hz}$ ,  $V_{IN} = 300 \text{ mVrms}$ , Gain = 26 dB)

### 3.2 Load Resistance

With a lower load resistance, the slew rate of the PWM switching is steep. While, for the higher load resistance, the slew rate is askew. Figure 7 shows two application cases: the first case is for a lower load resistance and the second case is for a higher load resistance. Then, the period of the low-level voltage (charging time for the bootstrap capacitors) in one cycle is actually longer with a lower load. So it is easier to cause the over-low voltage across the bootstrap capacitors with a higher load resistance.

 


Figure 7. Slew Rate of Output PWM

### 3.3 Input Signal Frequency

With a lower-frequency input signal, the duration is longer with high output than the high frequency input signal. For example, a 50-Hz sinewave input and 1-kHz sinewave input, as shown in Figure 8 and Figure 9. The duration of high output for 50-Hz input is 20 times that of 1-kHz input. Then the possibility of overdischarging on bootstrap capacitors with a 50-Hz input signal is a lot higher than the 1-kHz input.


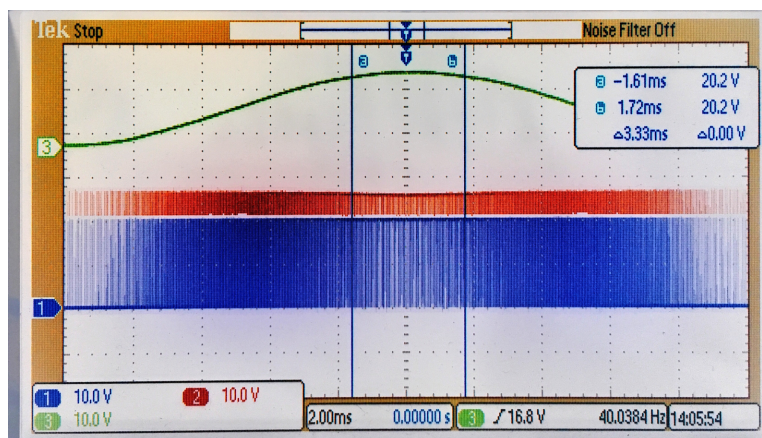


Figure 8. Output PWM With  $F_{IN} = 50 \text{ Hz}$   
(PVCC = 20 V, Open Load,  $F_{sw} = 1.2 \text{ MHz}$ ,  $V_{IN} = 600 \text{ mVrms}$ , Gain = 26 dB)

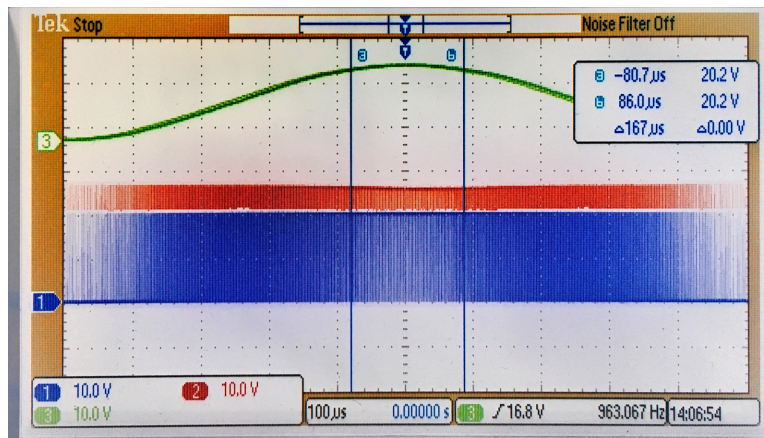


**Figure 9. Output PWM With  $F_{IN} = 1$  kHz (PVCC=20V, Open Load,  $F_{sw}=1.2$ MHz,  $V_{IN}=600$ mVrms, Gain=26dB)**

### 3.4 PVCC

A power MOSFET has capacitances between the gate-drain, gate-source, and drain-source terminals, which also contribute to the discharging on the bootstrap capacitors. When the high-side MOSFET is turned off, the voltage between gate-drain  $V_{gd}$  is  $-PVCC$ . When the high-side MOSFET is turned on,  $V_{gd}$  is changed to  $GVDD$  (the same as  $V_{gs}$ ). Then the charge that must be supplied to  $C_{gd}$  is as follows in Equation 1.

$$Q = C_{gd} \times (GVDD - (-PVCC)) = C_{gd} \times (GVDD + PVCC). \quad (1)$$

Therefore, more charge is needed for a higher PVCC, and then it is easier to cause overdischarging on the bootstrap capacitors with a higher PVCC.

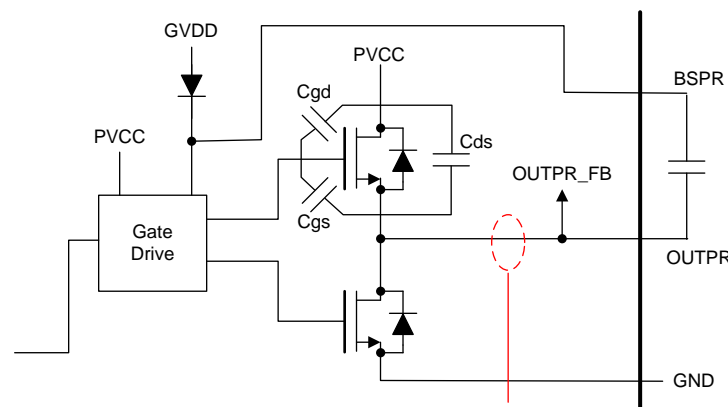

**Figure 10. Capacitance Equivalent Circuit**

Proper bootstrap capacitor selection and device configuration can drastically reduce these limitations. For extreme applications (large load and very low frequency input test signal), TI recommends using  $F_{sw} = 400$  kHz and 0.47- $\mu$ F bootstrap capacitors.

## 4 Conclusion

The bootstrap circuit is a very simple and low-cost solution for high-side MOSFET control on class-D audio amplifiers. Overdischarging on the bootstrap capacitors can occur in very extreme test cases. Using lower-frequency PWM settings (for example, 400 kHz) or a larger bootstrap capacitor (for example, 0.47  $\mu$ F) can avoid this issue.

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated